
## **PA system Matching Methods**


Purpose of Matching: To deliver maximum power from Amplifier to Loudspeaker.

Condition: Source resistance should be equal to load resistance.
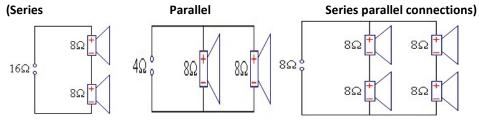
## <u>Impedance Matching – Normally Box speakers are connected</u>


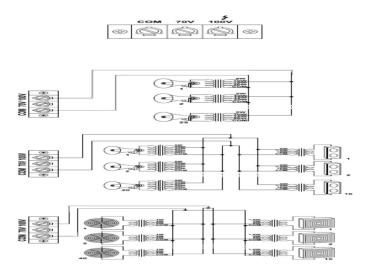
<u>Voltage Matching – To connect Horns and column Speakers. Line matching transformer should be available inside the spekers. (Parallel connection only)</u>



## **Amplifer Terminals:**

Mic : To connect Microphone Input
AUX : To connect Cassette Player Input
Line Out : To connect Booster Amplifier
Pre-Amp out : To connect Cassette Recorder